

1. a) $3.61 \angle 33.69^\circ$
- b) $3.61 \angle 56.31^\circ$
- c) $7.07 \angle 98.13^\circ$
- d) $7.07 \angle -8.13^\circ$
- e) $7.07 \angle -98.13^\circ$
- f) $7.07 \angle 81.87^\circ$
- g) $7.07 \angle 8.13^\circ$
- h) $7.07 \angle 171.87^\circ$

Use
 $|z| = \sqrt{x^2 + y^2}$
 and
 $\angle z = \tan^{-1}(y/x)$
 watch quadrants!

2. a) $6.58 + j2.39$
- b) $-6.58 - j2.39$
- c) $-6.58 - j2.39$
- d) $6.58 + j2.39$
- e) $2.82 + j1.03$
- f) $2.82 - j1.03$
- g) $10 + j0$
- h) $0 - j1$

Use Euler's equation
 $e^{j\theta} = \cos\theta + j\sin\theta$


3. a) $-4 + j$
- b) $3 + j$
- c) $-10 + 10j$
- d) $21.35 + j29.05$

4. a) $25.24 \angle 86.31^\circ$
- b) $4.12 \angle 165.96^\circ$
- c) $0.22 \angle 6.57^\circ$
- d) $.71 \angle 45^\circ$


5. a) $Z_{EQ} = 35 \Omega \leftarrow Z_{EQ} = 10 + 25$
- b) $= (10 - 1000j) \Omega \leftarrow Z_{EQ} = 10 + -j/\omega \cdot C$
- c) $= (10 + j) \Omega \leftarrow Z_{EQ} = 10 + j \cdot \omega \cdot L$
- d) $= (10 - j261.5) \Omega \leftarrow Z_{EQ} = 10 + -j/\omega C + j\omega L$
- e) $= (9.99 - j0.38) \Omega \leftarrow Z_1 = 10 \quad Z_2 = -j/\omega C \text{ in parallel}$
- f) $= (1.62 - j3.68) \Omega \leftarrow Z_1 = 10, Z_2 = -j/\omega C, Z_3 = j\omega L \text{ in parallel.}$

6. First write as impedances: $Z_R = 10 \Omega; Z_C = -j/(377 \cdot 10 \times 10^{-6})$
 $Z_L = j \cdot 377 \cdot 10 \times 10^{-3}$

note $V = 10 \angle 20^\circ$

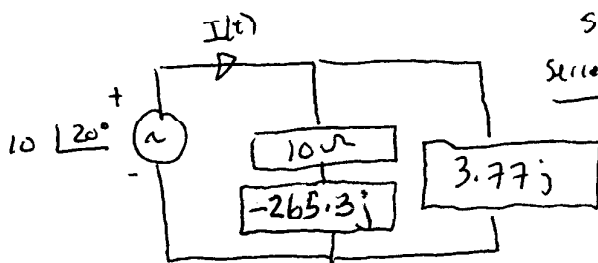

Simplify series/parallel

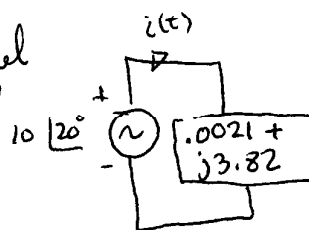

$$I = \frac{V}{Z}$$

$$= \frac{10 \angle 20^\circ}{.0021 + j3.82}$$

$$= 2.61 \angle -69.97^\circ$$

$$i(t) = 2.61 \cos(377t - 69.97^\circ) \text{ A}$$